

3-5

$$P_{\text{loss, cu}} = 20\text{W}$$

$$P_{\text{cu}} = I^2 R$$

$$\text{If } I \text{ is reduced by } 1/2, P_{\text{cu}} = \left(\frac{I}{2}\right)^2 R = \frac{I^2}{4} R = \frac{20\text{W}}{4} = \boxed{5\text{W}}$$

P_{cu} would be reduced to $1/4$ of previous loss

3-7

$$P_{\text{in}} = 1250\text{W} \quad \eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{in}} - (P_{\text{cu}} + P_{\text{core}})}{P_{\text{in}}}$$

$$P_{\text{cu}} = 22\text{W}$$

$$P_{\text{core}} = 13\text{W}$$

$$\eta = \frac{1250\text{W} - (22\text{W} + 13\text{W})}{1250\text{W}} = \boxed{.972 \text{ of } 97.2\%}$$

3-10

$$V_{\text{HS}} = 240\text{V}$$

$$V_{\text{LS}} = 120\text{V}$$

$$S_{\text{rated}} = 10\text{KVA}$$

$$R_L = 10\Omega$$

A) find I_{LS} ,
$$I_{\text{LS}} = \frac{V_{\text{LS}}}{R_L} = \frac{120\text{V}}{10\Omega} = \boxed{12\text{A}}$$


B) find I_{HS} ,
$$\frac{V_{\text{HS}}}{V_{\text{LS}}} = \frac{I_{\text{LS}}}{I_{\text{HS}}} \quad I_{\text{HS}} = \frac{I_{\text{LS}} V_{\text{LS}}}{V_{\text{HS}}} = \frac{12\text{A} \cdot 120\text{V}}{240\text{V}} = \boxed{6\text{A}}$$

C) find real input power (P_{in}),
$$P_{\text{in}} = P_{\text{out}}$$

$$V_1 I_1 = V_2 I_2$$

$$P_{\text{in}} = V_1 I_1 = 240\text{V} \cdot 6\text{A} = \boxed{1440\text{W}}$$

D) reflect R_L on xfmr LS

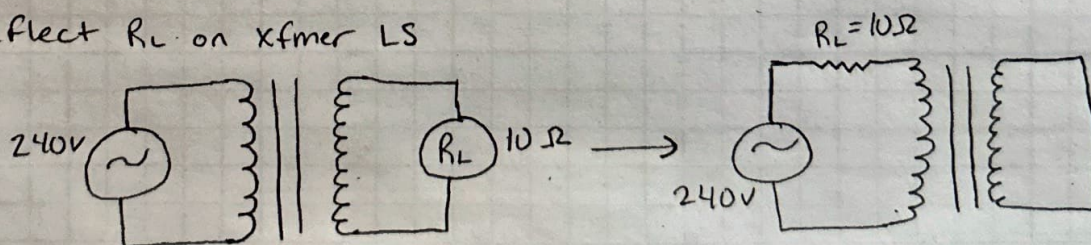

3-12 xfmer $\rightarrow$ 3KVA

$$V_T = 120V$$

$$I_0 = 1.5A$$

$$P = 33W$$

A) Find I_{fe} , $I_{fe} = \frac{P}{V_T} = \frac{33VA}{120V} = \boxed{.275A \text{ or } 275mA}$

B) Find R_{fe} , $R_{fe} = \frac{V_T}{I_{fe}} = \frac{120V}{.275A} = \boxed{436.36 \Omega}$

C) if $I_{fe} = .625A$, find I_m ,

$$I_m = \sqrt{I_0^2 - I_{fe}^2} = \sqrt{1.5^2 - .625^2} = \boxed{1.36A}$$

D) if $I_m = 2.2A$, find X_m

$$X_m = \frac{V_T}{I_m} = \frac{120V}{2.2A} = \boxed{54.54 \Omega}$$