

1) if $a = 6$, find V_L $V_L = V_{pri} + V_{sec}$
 $V_i = 240V$

$$V_{sec}: a = \frac{V_{HS}}{V_{LS}} = \frac{V_i}{V_{sec}}$$

$$V_{sec} = \frac{V_i}{a} = \frac{240V}{6} = 40V$$

$$V_L = 240V + 40V = \boxed{280V}$$

2) If $V_L = 120V$, ^{find} total power delivered to load
 $I_L = 5A$

$$S_{load} = V_L \cdot I_L = 120V \cdot 5A = \boxed{600VA}$$

3) if $I_{Tr} = 5A$, find output current I_L
 $I_{cond} = 20A$

$$I_{cond} = I_{sec} = I_L = \boxed{20A}$$

4) if $I_{Tr} = 50A$, find I_i (input current)
 $I_{cond} = 125A$

$$I_i = I_{Total} = I_{pri} + I_{sec} = I_{Tr} + I_{cond} = 125A + 50A = \boxed{175A}$$

5) $V_{HS} (Rated) = 480V$

$V_{LS} (rated) = 120V$

$S_{rated} = 10KVA$

, if operated @ rated voltage + load,

find I_i

$$S_{rated} = V_{pri} I_{pri} = V_{sec} I_{sec}$$

$$V_i I_{Tr} = V_L I_{cond}$$

$$I_{cond} = \frac{S_{rated}}{V_L} = \frac{10000VA}{120V} = 83.3A$$

$$I_{Tr} = \frac{S_{rated}}{V_i} = \frac{10000VA}{480V} = 20.83A$$

$$I_i = I_{Tr} + I_{cond} = 83.3A + 20.83A = \boxed{104A}$$

6) If $V_{in} = 100V$, find turns ratio a
 $V_{out} = 5V$

$$a = \frac{V_{Hs}}{V_{Ls}} = \frac{V_{in} - V_{out}}{V_{out}} = \frac{100V - 5V}{5V} = \boxed{19}$$

7). If $P_{out} = 600VA$, find I_{in}
 $V_{in} = 60V$

$$P_{out} = P_{in} = 600VA$$

$$P_{in} = V_{in} I_{in} \quad I_{in} = \frac{P_{in}}{V_{in}} = \frac{600VA}{60V} = \boxed{10A}$$